

Name:

**Aim**


To make a switch and put it in the circuit so that you can turn the light on and off.

**Apparatus:**


Strip of cardboard  
Brads  
Battery  
Paper clip

Bulb  
Rubber band  
Alligator clips


**Method:**

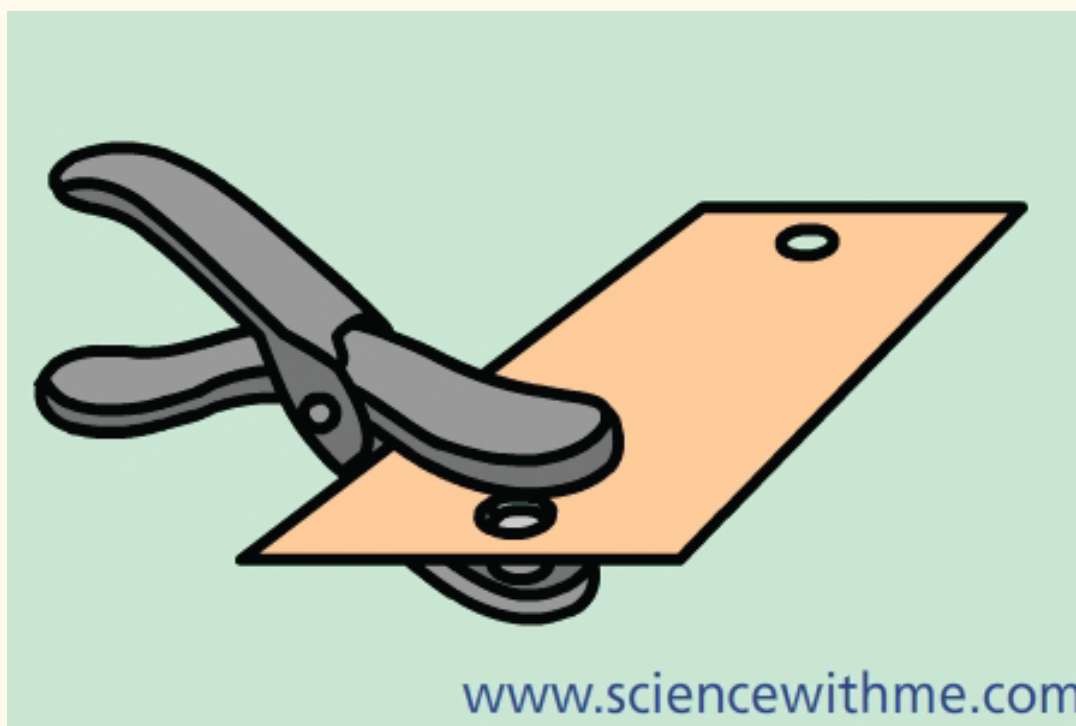

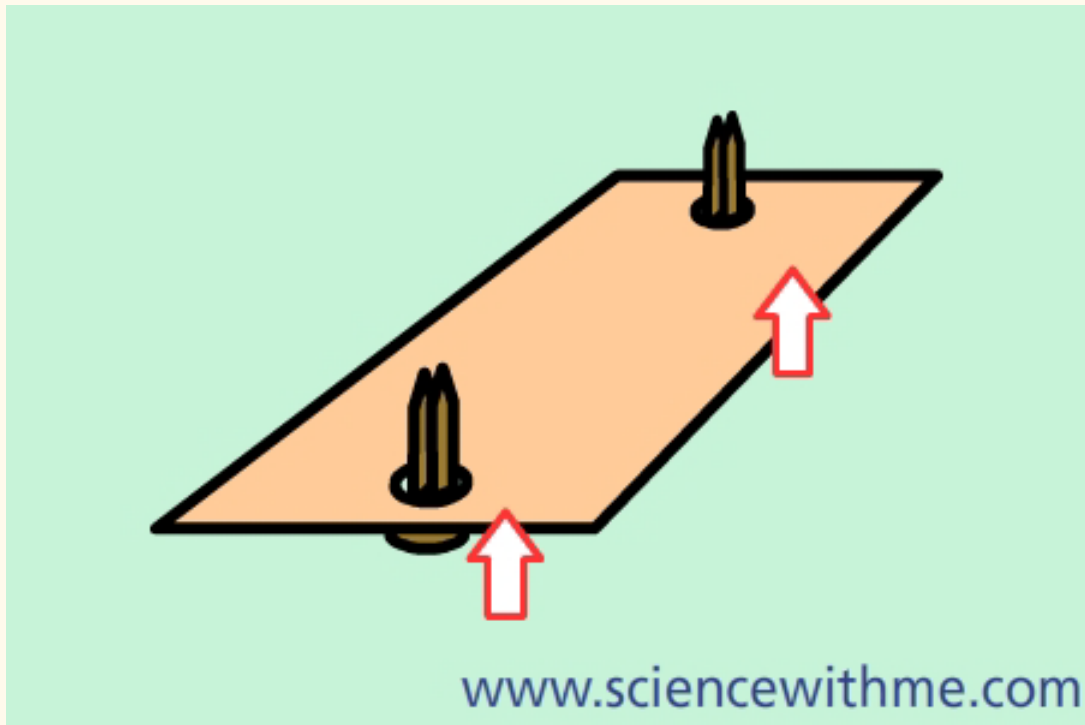
Step 1: Punch two holes in the cardboard.



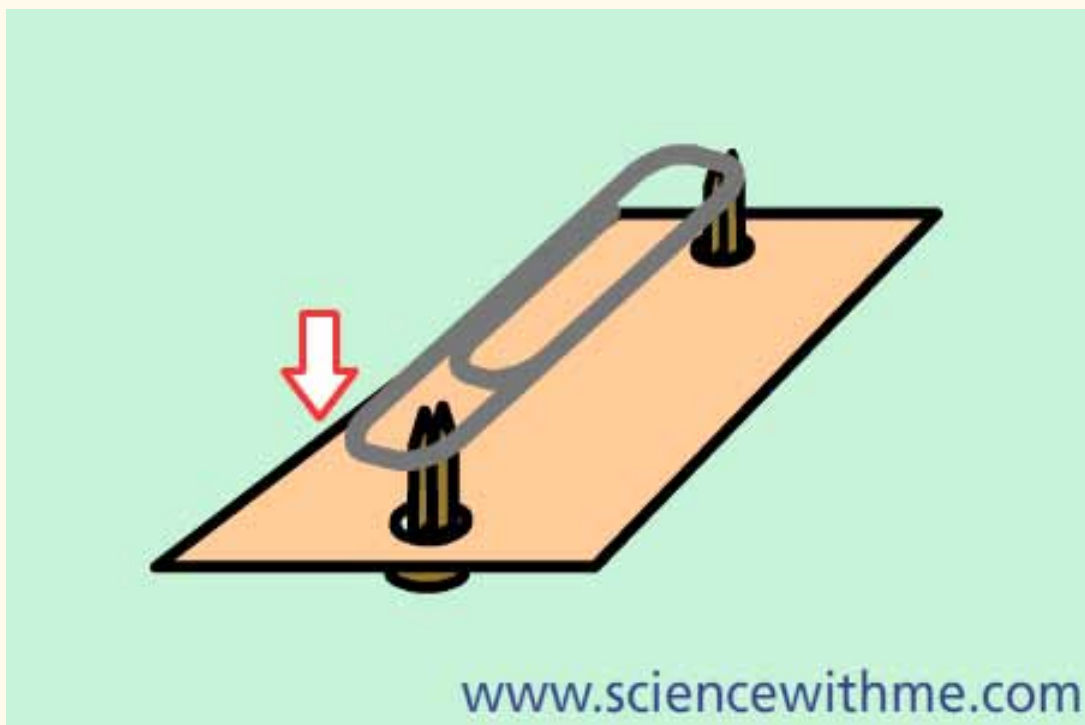**Step 2:** Push two metal brads through the pre-punched holes.




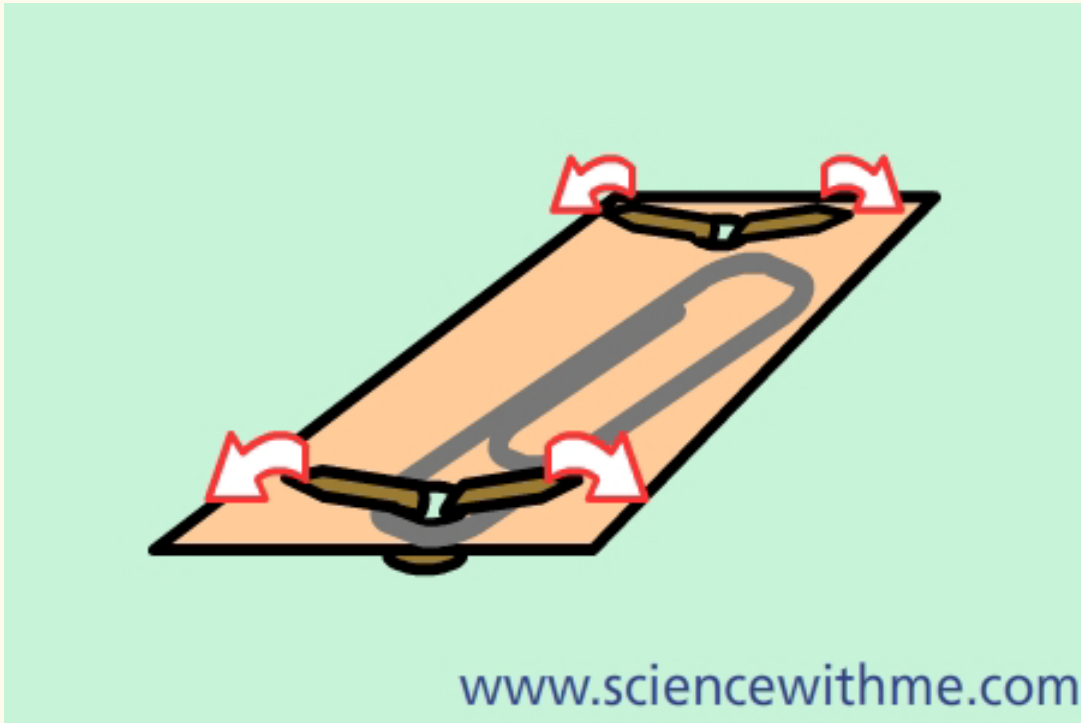**Step 3:** Place the paper clip over one of the brads.




[www.sciencewithme.com](http://www.sciencewithme.com)

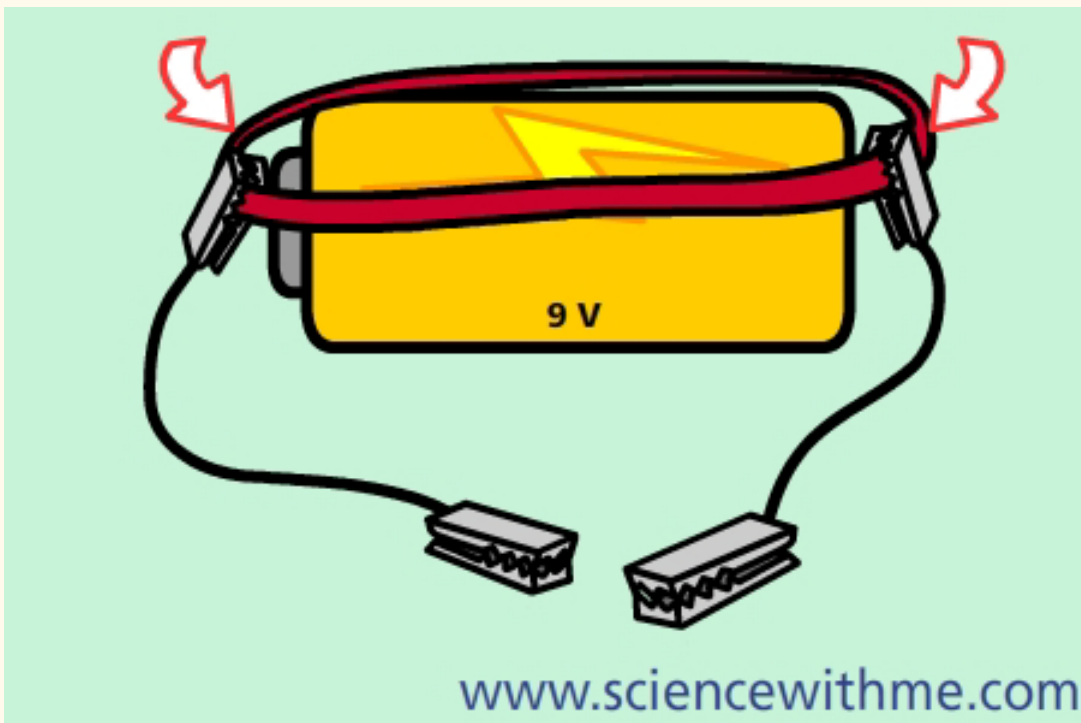**Step 4:** Lock the paper clip in place by bending open the braid on the underside. Bend open the other braid too.




[www.sciencewithme.com](http://www.sciencewithme.com)

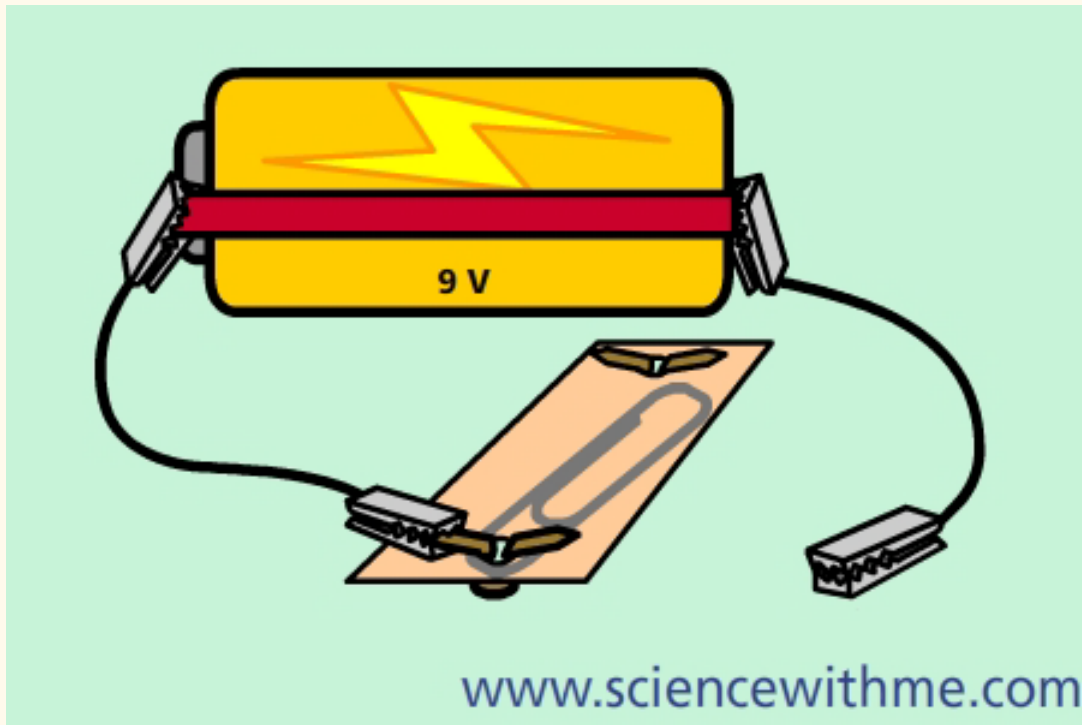
**Step 5:** Place a rubber band around the battery and connect the alligator clips to the each end of the battery.



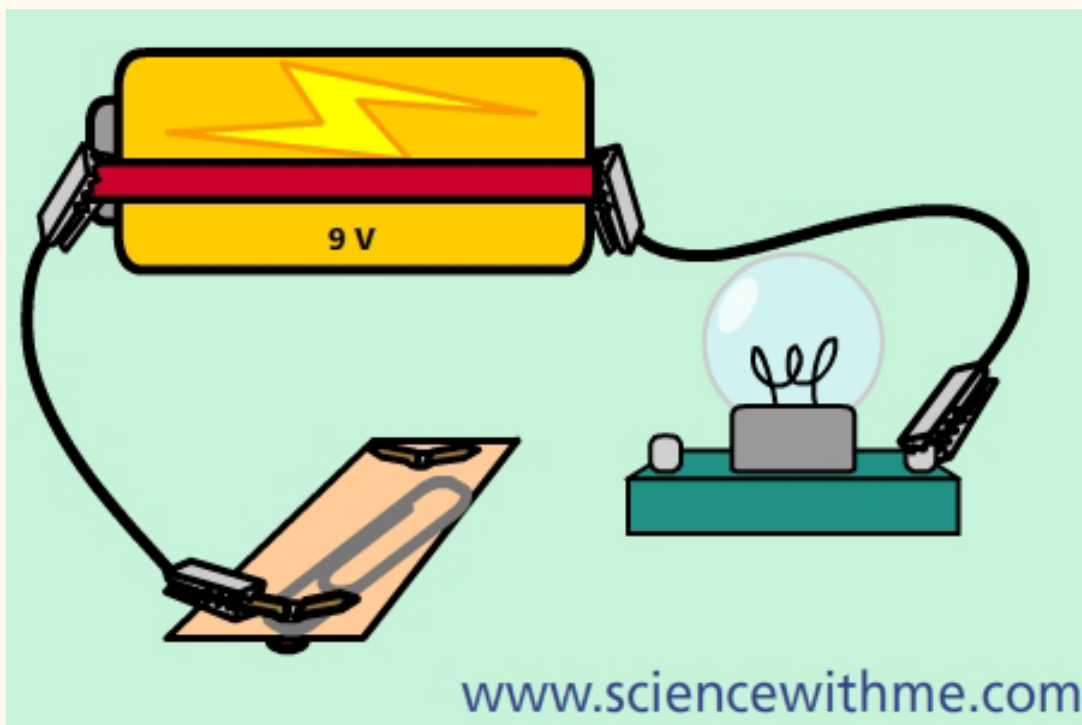
**Step 6:** Connect one of the alligator clips to the switch.



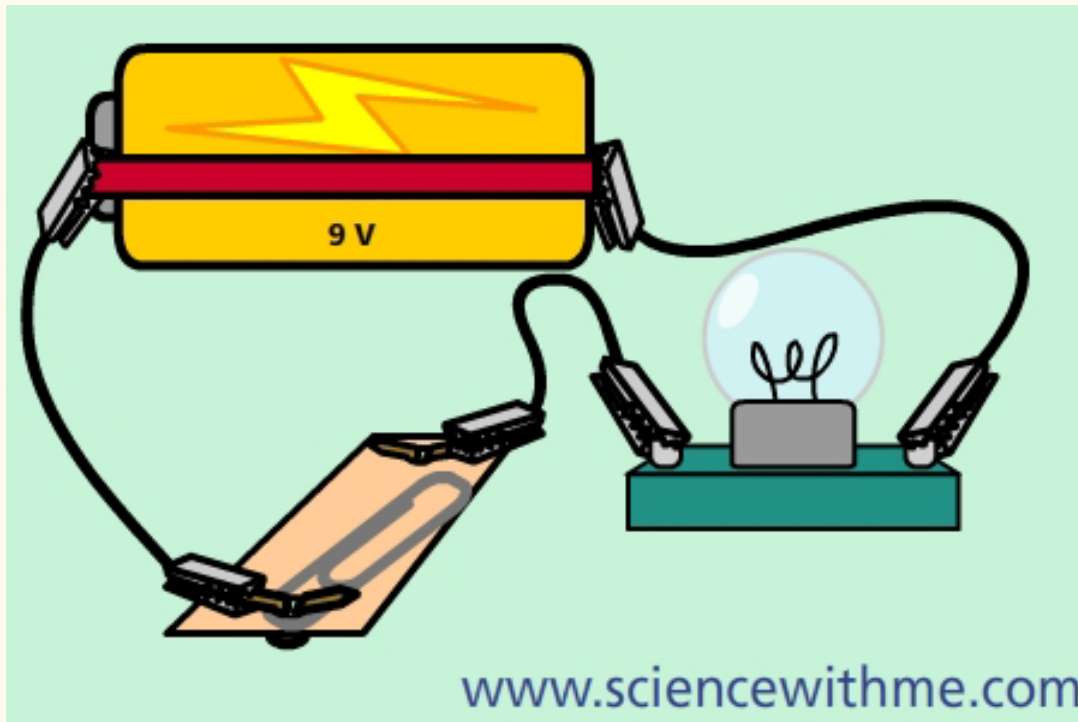
**Step 7:** Connect the other alligator clip to the bulb.



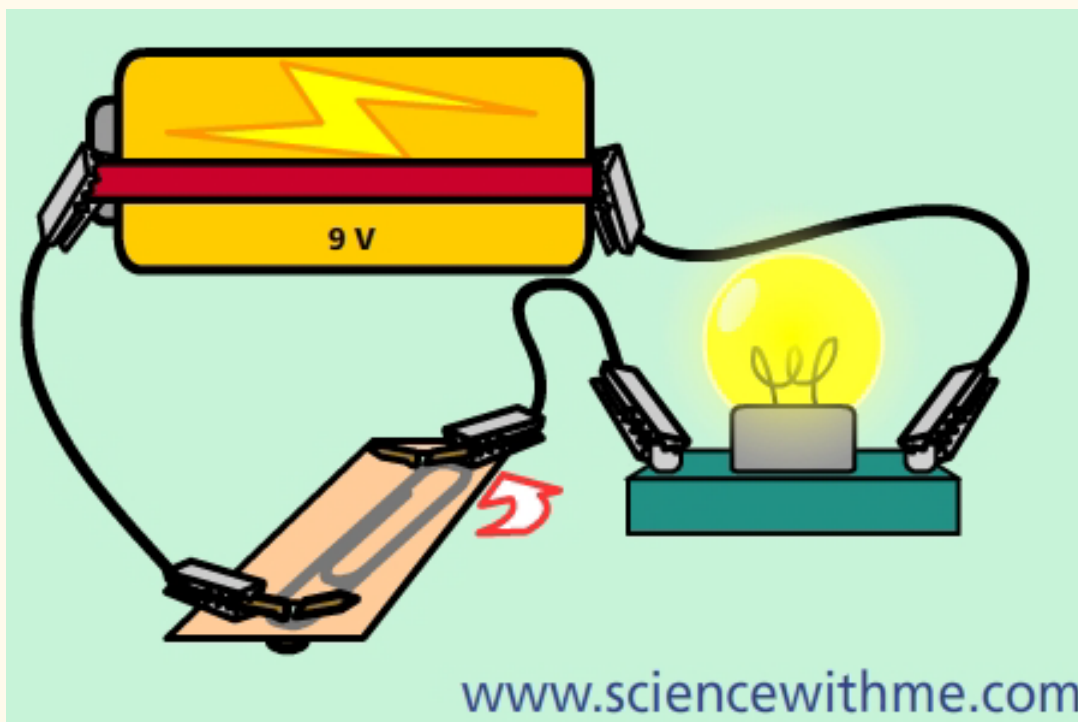Step 8: Connect a third alligator clip to the second braid of the switch and the second metal connector on the light bulb.



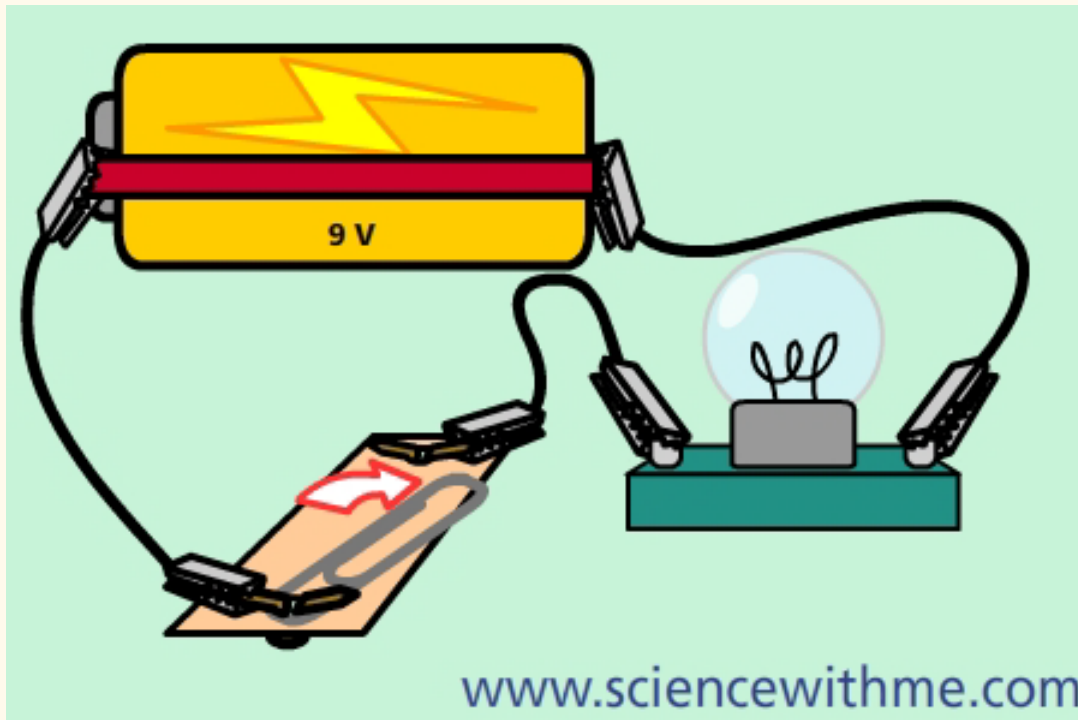Step 9: What happens when you push the paper clip against the metal brad and CLOSE the circuit?  
Circle your answer below:  
The light turns                      ON                      OFF



Step 10: What happens when you pull the paper clip away from the metal braid and OPEN the circuit?

Circle your answer below:

The light turns

ON

OFF